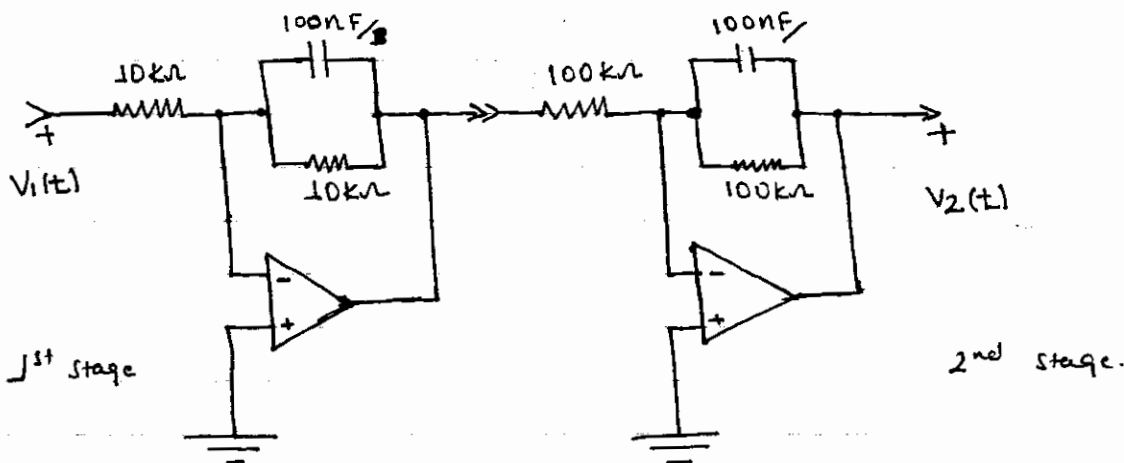




# ECE 301, H.W AG

October 20, 06

11-9  
16/10



Qn. find the Voltage transfer function  $T_V(s) = \frac{V_2(s)}{V_1(s)}$ .

For the 1<sup>st</sup> Stage.

$$Z_2(s) = \frac{1}{10^7 s + \frac{1}{10^4}} = \frac{10^7}{(s+1000)}$$

and

$$Z_1(s) = 10^4$$

$$\therefore T_{V1}(s) = \frac{-Z_2}{Z_1} = \frac{-1000}{s+1000}$$

For the 2<sup>nd</sup> Stage.

$$Z_2(s) = \frac{1}{10^7 s + \frac{1}{10^5}} = \frac{10^7}{(s+100)}$$

and

$$Z_1(s) = 10^5$$

$$\therefore T_{V2}(s) = \frac{-Z_2}{Z_1} = \frac{-100}{s+100}$$

Using the Chain rule:

$$T_V(s) = T_{V1}(s) \cdot T_{V2}(s) = \left( \frac{-1000}{s+1000} \right) \cdot \left( \frac{-100}{s+100} \right)$$

$$T_V(s) = \frac{10^5}{(s+100)(s+1000)}$$

⇒  $T_V(s)$  has poles at  $s = -100$  and  $s = -1000$  and a double zero at infinity.