

ECE 301


HW A7

Due 10/23/06



11.14)

10

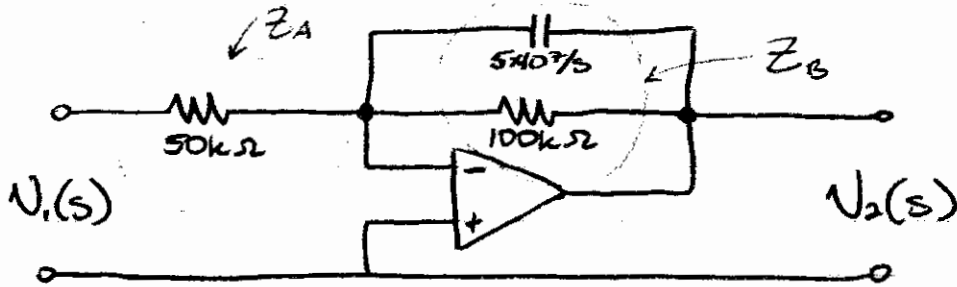

Assuming ideal op-amp, $Z_{in} = 50k\Omega$ and $Z_{out} = 0$

$$\frac{N_2(s)}{N_1(s)} = -\frac{Z_B}{Z_A} \rightarrow Z_B = 10^5 / (5 \times 10^7/s) \rightarrow Z_A = 50000$$

$$= \frac{5 \times 10^{12}/s}{10^5 + 5 \times 10^7/s} \cdot \frac{s/10^5}{s/10^5}$$

$$= \frac{5 \times 10^7}{s + 5 \times 10^2}$$

$$\frac{N_2(s)}{N_1(s)} = T(s) = \frac{-1000}{s + 500}$$

$$Y(s) = T(s)/s = \frac{-1000}{s(s + 500)}$$

p: 0, -500
z: none

$$k_1 = \frac{-1000}{500} = -2$$

$$k_2 = \frac{-1000}{-500} = 2$$

$$Y(s) = \frac{-2}{s} + \frac{2}{s + 500}$$

$$y(t) = [-2 + 2e^{-500t}]u(t)$$