

ECE 301
Homework A8

20/20

11-21 $h(t) = 1000 [e^{-1000t}] u(t)$

$x(t) = 5t u(t)$

10

$H(s) = \frac{1000}{s+1000}$

$X(s) = \frac{5}{s^2}$

$Y(s) = \frac{5000}{s^2(s+1000)}$
 $= \frac{1}{s} \left(\frac{5000}{s+1000} \right)$
 $= \frac{1}{s} \left(\frac{k_1}{s} + \frac{k_2}{s+1000} \right)$


$k_1 = 5, k_2 = -5$

$Y(s) = \frac{5}{s^2} + \frac{5}{s(s+1000)}$
 $= \frac{5}{s^2} - \left(\frac{k_{21}}{s} + \frac{k_{22}}{s+1000} \right)$
 $= \frac{5}{s^2} - \left(\frac{1}{200s} - \frac{1}{200(s+1000)} \right)$
 $= \frac{5}{s^2} - \frac{1/200}{s} + \frac{1/200}{s+1000}$

$y(t) = \left(5t - \frac{1}{200} + \frac{1}{200} e^{-1000t} \right) u(t)$

11-29 $i_1(t) = 5 \cos 1000t \text{ mA}$

10

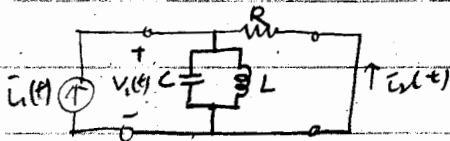

$T(s) = \frac{1/R}{Cs + 1/s + R}$
 $= \frac{1/s}{RLCs^2 + Ls + R}$
 $|T(j\omega)| = \frac{L\omega}{-RL\omega^2 + jL\omega + R}$
 $= \frac{-L\omega}{RL\omega^2 - jL\omega - R}$

$\omega = 1000$

$T(j1000) = \frac{2000j}{2000 \times 500 \times 10^{-9} (1000)^2 - 2000j - 1000}$
 $= \frac{j}{1 - 2j}$
 $= -1$

$i_{2AS}(t) = -5 \cos(1000t) \text{ mA}$

when $\omega = 2000$

$T(j2000) = \frac{4000j}{2000 \times 500 \times 10^{-9} (2000)^2 - 4000j - 1000} = \frac{4j}{3-4j} = \frac{4e^{j90^\circ}}{5e^{-j53.13^\circ}}$

$$T(j2000) = 0.8 \angle 143.13^\circ$$

$$\begin{aligned} i_{LSS}(t) &= 10 \times 0.8 \cos(2000t + 143.13^\circ) \\ &= 8 \cos(2000t + 143.13^\circ) \text{ mA} \end{aligned}$$