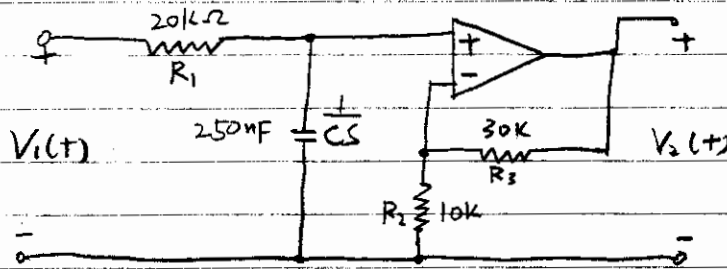


12-3



$R_1 = 20k$

$R_2 = 10k$

$R_3 = 30k$

$C = 250nF$


10

$$\Rightarrow \frac{\frac{1}{Cs}}{R_1 + \frac{1}{Cs}} = \frac{1}{R_1 Cs + 1}$$

$$\Rightarrow T_V(s) = \left[\frac{1}{R_1 Cs + 1} \right] \cdot \left[\frac{R_3 + R_2}{R_2} \right] = \frac{R_3 + R_2}{R_1 R_2 Cs + R_2} = \frac{40000}{50s + 10000}$$

$$= \frac{800}{s + 200}$$

a) $|T_V(0)| = 4$; $|T_V(\infty)| = 0$, $\omega_c = 200 \text{ rad/s}$, Low-pass

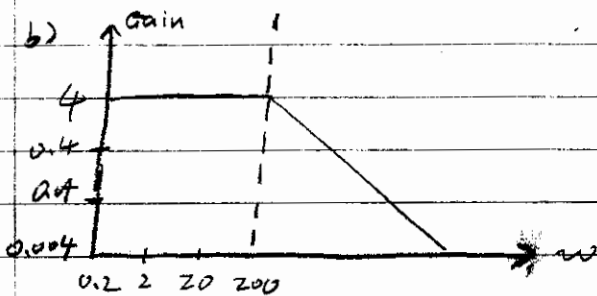

$$0) \frac{R_3 + R_2}{R_1 R_2 Cs + R_2} \Big|_{s=0} = \frac{R_3 + R_2}{R_2}$$

$$\Rightarrow \begin{cases} R_3 + R_2 = 10 \\ R_2 = 1 \end{cases} \quad \text{Since } R_2 = 10k, \text{ change } R_3 = 90k$$