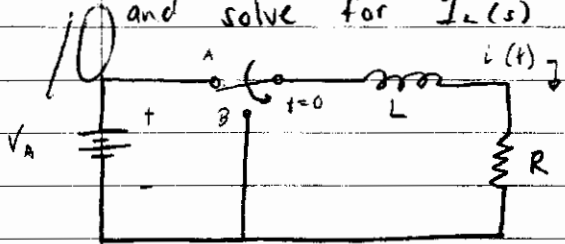



Ch. 10 (11, 17, 23, 25, 26)

50/50


11 The switch in Figure P10-11 has been in position A for a long time and is moved to position B at  $t=0$ . Transform the circuit into the  $s$  domain and solve for  $I_L(s)$  and  $i_L(t)$  in symbolic form.



Initial conditions

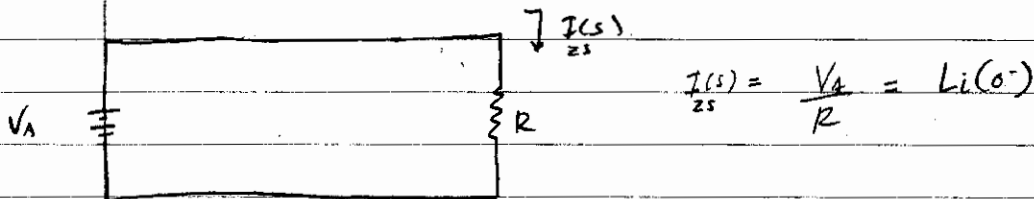

$t > 0$

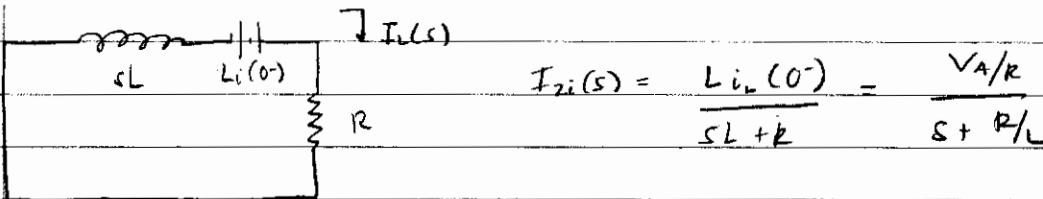


$$I_L(s) = \frac{V_A/R}{s + R/L}$$

$$i_L(t) = \left[ \frac{V_A}{R} e^{-(R/L)t} \right] u(t)$$

17 The switch in Figure P10-17 has been in position A for a long time and is moved to position B at  $t=0$

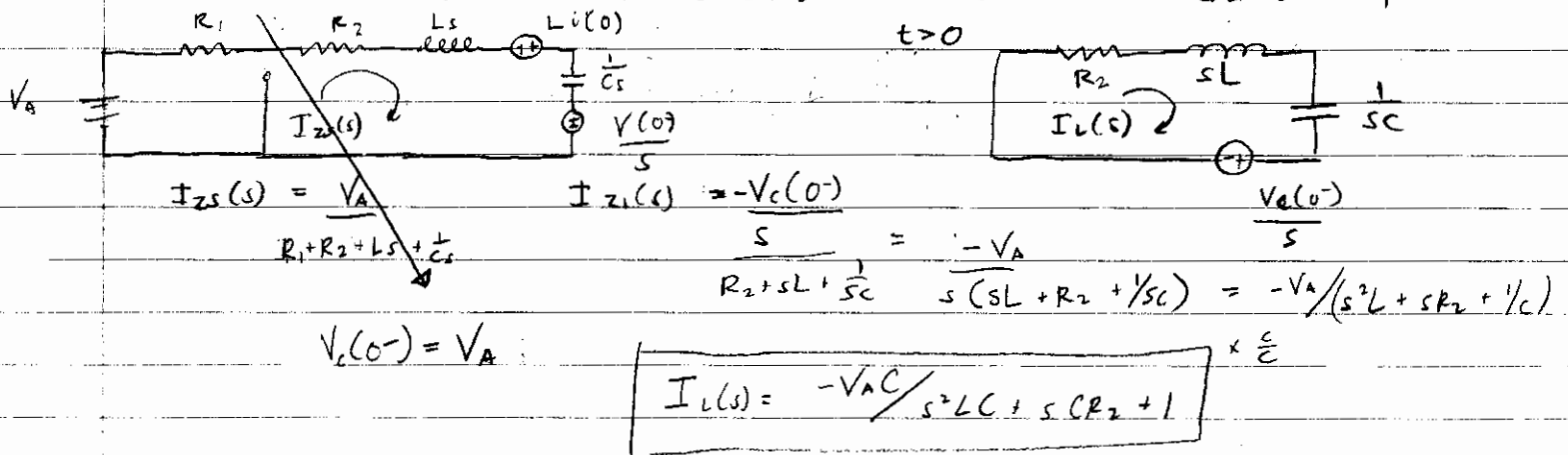10 (a) Transform the circuit into the  $s$  domain and solve for  $I_L(s)$  in symbolic form.



(b) Find  $i_L(t)$  for  $R_1 = R_2 = 500 \Omega$ ,  $L = 250 \text{ mH}$ ,  $C = 4 \mu\text{F}$  and  $V_A = 15 \text{ V}$


$$I_L(s) = \frac{-V_A C}{LCs^2 + R_2 C s + 1} = \frac{-V_A/L}{s^2 + \frac{R_2}{L} s + 1/LC}$$

$$I_L(s) = \frac{-60}{s^2 + 2ks + 1000k}$$

$$\frac{1}{(s+\alpha)^2} \quad I_L(s) = \frac{-60}{(s+1000)^2}$$

$$i_L(t) = -[60t e^{-1000t}] u(t) \text{ A}$$

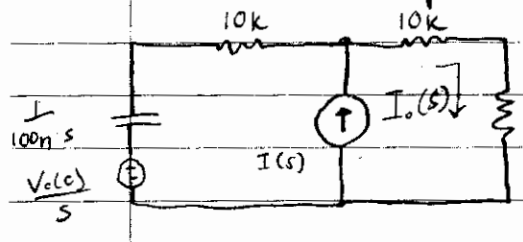23 There is no energy stored in the capacitor at  $t=0$ . Transform the circuit into the  $s$  domain and use current division to find  $V_o(t)$  when the input is  $i_s(t) = 2.5 e^{-100t} u(t) \text{ mA}$ . Identify the forced and natural poles in  $V_o(s)$



$$I_s(s) = \frac{2.5}{s+100}$$

$$V_o(s) = \frac{10k + \frac{1000k}{s}}{25k + \frac{1000k}{s}} \cdot \frac{2.5}{s+100} = \frac{25ks + 25000k}{25ks^2 + 12500s + 1,000,000k} \cdot \frac{2.5}{s+100}$$

$$= \frac{s+1000}{s^2 + 500s + 40000} = \frac{s+1000}{(s+400)(s+100)}$$

$$I_o(s) = \frac{k_1}{s+400} + \frac{k_2}{s+100}$$

$p_1 = -400$   
 $p_2 = -100$

$$k_1 = -2 \quad k_2 = 3$$

$$I_o(s) = [-2e^{-400t} + 3e^{-100t}] u(t) \text{ mA}$$



$$V_o(s) = I_o(s) 5k$$

$$V_o(s) = [-10e^{-400t} + 15e^{-100t}] u(t) \text{ V}$$

$I$  passive sign from source

$p_1 = -400$  natural pole  $p_2 = -100$  forced pole

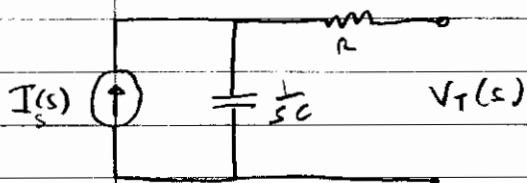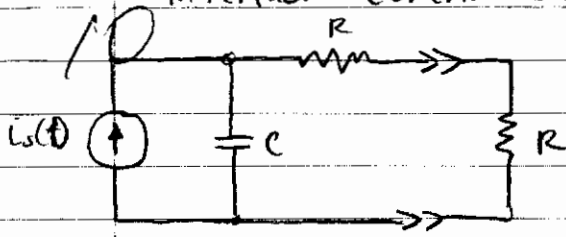
25 The circuit is in the zero state. Use a Thevenin equivalent to find the s-domain relationship between the input  $I_s(s)$  and the interface current  $I(s)$



$$V_T(s) = I_s(s) \cdot \frac{1}{sC}$$

$$I_{sc} = \frac{\frac{1}{sC} I_s(s)}{R + \frac{1}{sC}} = \frac{I_s(s)}{sCR + 1}$$

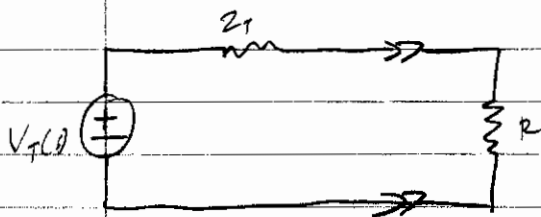
$$Z_T = \frac{V_T(s)}{I_{sc}(s)} = \frac{I_s(s)/sC}{I_s(s)} = \frac{sCR + 1}{sC}$$



$$I(s) = \frac{V_T(s)}{Z_T + R} = \frac{V_T(s)}{\frac{sCR + 1}{sC} + R} = \frac{I_s(s) \cdot \frac{1}{sC}}{\frac{sCR + 1 + sCR}{sC}} = \frac{I_s(s) \cdot \frac{1}{sC}}{\frac{2sCR + 1}{sC}}$$

$$I(s) = \frac{1}{2sCR + 1} I_s(s)$$

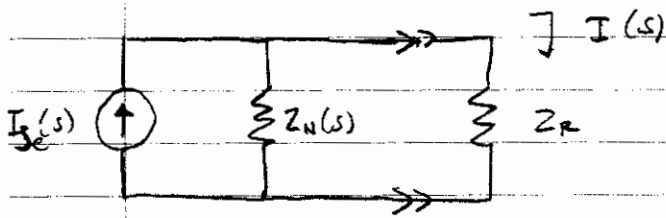26 Repeat Problem 25 using a Norton equivalent circuit.



$$I_{sc}(s) = \frac{I(s)}{\frac{s}{sCR+1}}$$

10

$$I(s) = \frac{Z_N(s)}{Z_R + Z_N(s)} I_{sc}(s)$$

$$Z_N = \frac{sCR+1}{sC}$$

$$I(s) = \left[ \frac{\frac{sCR+1}{sC}}{\frac{sCR+1}{sC} + R} * \frac{I_{sc}(s)}{sCR+1} \right]$$

$$= \frac{sCR+1/sC}{\frac{sCR+1}{sC} + R} * \frac{I_{sc}(s)}{sCR+1}$$

$$= \frac{sCR+1}{sC} \cdot \frac{sC}{2sCR+1} \cdot \frac{I_{sc}(s)}{sCR+1}$$

$$I(s) = \frac{1}{2sCR+1} I_{sc}(s)$$