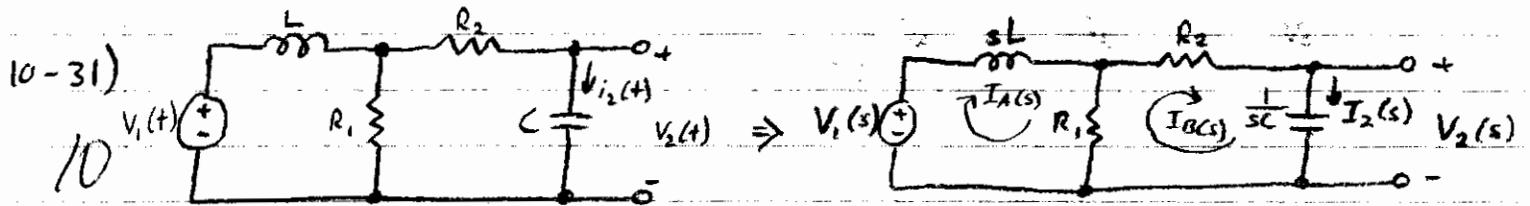


ECE 301 B3 40/40

10/18/06



There is no initial energy

A) Transform circuit into s-domain and find mesh-current eq.

$$sL I_A(s) + R_1 (I_A(s) - I_B(s)) - V_1(s) = 0$$

$$R_2 I_B(s) + \frac{1}{Cs} I_B(s) + R_1 (I_B(s) - I_A(s)) = 0 \quad I_B(s) = I_2(s)$$

$$\begin{aligned} (sL + R_1) I_A(s) - R_1 I_2(s) &= V_1(s) \\ -R_1 I_A(s) + (R_2 + \frac{1}{Cs} + R_1) I_B(s) &= 0 \end{aligned}$$

B)
$$\begin{bmatrix} sL + R_1 & -R_1 \\ -R_1 & R_2 + \frac{1}{Cs} + R_1 \end{bmatrix} \begin{bmatrix} I_A(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} V_1(s) \\ 0 \end{bmatrix}$$

$$A_2(s) = \begin{bmatrix} sL + R_1 & V_1(s) \\ -R_1 & 0 \end{bmatrix} = -R_1 V_1(s)$$

$$\begin{aligned} \Delta(s) &= \begin{vmatrix} sL + R_1 & -R_1 \\ -R_1 & R_2 + \frac{1}{Cs} + R_1 \end{vmatrix} = R_2 L s + R_1 R_2 + \frac{L}{C} + \frac{R_1}{Cs} + R_1 L s + R_1^2 - R_1^2 \\ &= R_2 L (Cs^2 + R_1 R_2 (Cs + Ls + R_1) + R_1 L Cs^2) \\ &= (R_1 + R_2) L Cs^2 + (R_1 R_2 (C + L)) s + R_1 \end{aligned}$$

$$I_2(s) = \frac{A_2(s)}{\Delta(s)} = \frac{R_1 C s V_1(s)}{(R_1 + R_2) L C s^2 + (R_1 R_2 (C + L)) s + R_1}$$

C) Find $i_2(t)$ for $v_1(t) = 100 u(t) V$, $R_1 = 1 k\Omega$, $R_2 = 2 k\Omega$, $L = 4 H$, $C = 500 nF$


$$I_2(s) = \frac{1/20}{\frac{3}{500} s^2 + 5s + 1000} = \frac{25}{3s^2 + 2500s + 500000} = \frac{25}{(s+500)(3s+1000)}$$

$$p_1 = -500 \quad K_1 = \frac{25}{3(-500) + 1000} = -\frac{1}{20} \quad p_2 = -\frac{1000}{3} \quad K_2 = \frac{25}{-\frac{1000}{3} + 500} = \frac{3}{20}$$

$$I_2(s) = \frac{-1/20}{s+500} + \frac{1/20}{s+1000/3}$$

$$i_2(t) = \left[-\frac{1}{20} e^{-500t} + \frac{1}{20} e^{-1000t/3} \right] u(t) \text{ A}$$
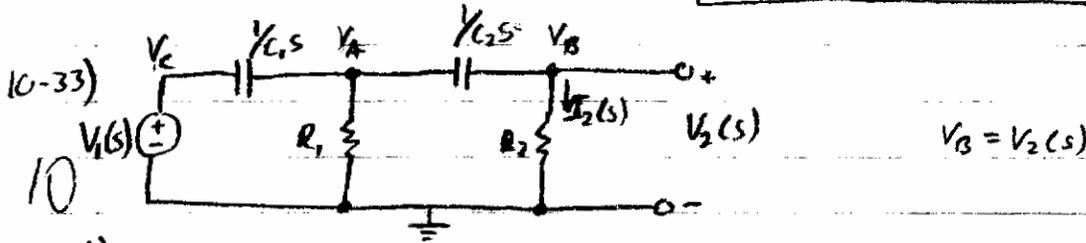
$$i_2(t) = \left[-50 e^{-500t} + 50 e^{-1000t/3} \right] u(t) \text{ mA}$$



A)

$$\text{Node A: } (C_1 s + 1/R_1 + C_2 s) V_A - C_2 s V_2(s) = C_1 s V_1(s)$$

$$\text{Node B: } (C_2 s + 1/R_2) V_2(s) - C_2 s V_A = 0$$

B)

$$\begin{bmatrix} C_1 s + 1/R_1 + C_2 s & -C_2 s \\ -C_2 s & C_2 s + 1/R_2 \end{bmatrix} \begin{bmatrix} V_A \\ V_2(s) \end{bmatrix} = \begin{bmatrix} C_1 s V_1(s) \\ 0 \end{bmatrix}$$

$$\Delta_2(s) = \begin{bmatrix} C_1 s + 1/R_1 + C_2 s & C_1 s V_1(s) \\ -C_2 s & 0 \end{bmatrix} = C_1 C_2 s^2 V_1(s)$$

$$\Delta(s) = \begin{bmatrix} C_1 s + 1/R_1 + C_2 s & -C_2 s \\ -C_2 s & C_2 s + 1/R_2 \end{bmatrix} = C_1 C_2 s^2 + \frac{C_2 s}{R_1} + \frac{C_2 s}{R_2} + \frac{1}{R_1 R_2} + \frac{C_1 s}{R_2}$$

$$= R_1 R_2 C_1 C_2 s^2 + R_2 C_2 s + R_1 C_2 s + 1 + R_1 C_1 s$$

$$= \frac{R_1 R_2 C_1 C_2 s^2 + (R_2 C_2 + R_1 C_2 + R_1 C_1) s + 1}{R_1 R_2}$$

$$V_2(s) = \frac{\Delta_2(s)}{\Delta(s)} = \frac{R_1 R_2 C_1 C_2 s^2 V_1(s)}{R_1 R_2 C_1 C_2 s^2 + (R_1 C_1 + R_2 C_2 + R_1 C_2) s + 1}$$


c) $V_2(s) = \frac{.003s}{.0001s^2 + .025s + 1} = \frac{30s}{s^2 + 250s + 10000} = \frac{30s}{(s+50)(s+200)}$

$$p_1 = -50 \quad k_1 = \frac{30(-50)}{-50+200} = -10$$

$$p_2 = -200 \quad k_2 = \frac{30(-200)}{-200+50} = 40$$

$$V_2(s) = \frac{40}{s+200} - \frac{10}{s+50}$$
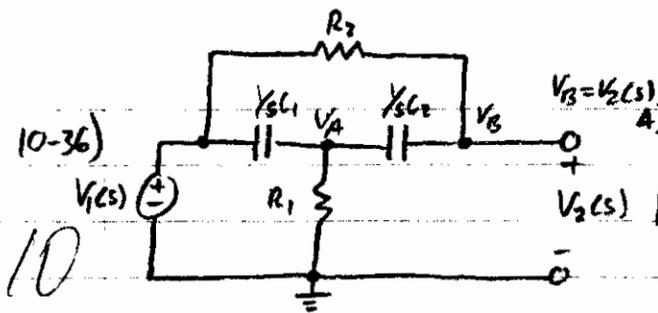
$$V_2(t) = \left[40 e^{-200t} - 10 e^{-50t} \right] u(t) \text{ V}$$



Node A: $(C_1 s + \frac{1}{R_1} + C_2 s) V_A - C_2 s V_2(s) = C_1 s V_1(s)$
 Node B: $(\frac{1}{R_2} + C_2 s) V_2(s) - C_2 s V_A = \frac{V_1(s)}{R_2}$

$$b) \begin{bmatrix} C_1 s + \frac{1}{R_1} + C_2 s & -C_2 s \\ -C_2 s & \frac{1}{R_2} + C_2 s \end{bmatrix} \begin{bmatrix} V_A \\ V_2(s) \end{bmatrix} = \begin{bmatrix} C_1 s V_1(s) \\ V_1(s)/R_2 \end{bmatrix}$$

$$\Delta_2(s) = \begin{bmatrix} C_1 s + \frac{1}{R_1} + C_2 s & C_1 s V_1(s) \\ -C_2 s & V_1(s)/R_2 \end{bmatrix} = \frac{C_1 s V_1(s)}{R_2} + \frac{V_1(s)}{R_1 R_2} + \frac{C_2 s V_1(s)}{R_2} + C_1 C_2 s^2 V_1(s)$$

$$= \frac{R_1 C_1 s V_1(s) + V_1(s) + R_1 C_2 s V_1(s) + R_1 R_2 C_1 C_2 s^2 V_1(s)}{R_1 R_2}$$

$$\Delta(s) = \begin{bmatrix} C_1 s + \frac{1}{R_1} + C_2 s & -C_2 s \\ -C_2 s & \frac{1}{R_2} + C_2 s \end{bmatrix} = \frac{C_1 s}{R_2} + \frac{1}{R_1 R_2} + \frac{C_2 s}{R_2} + C_1 C_2 s^2 + \frac{C_2 s}{R_1} + \frac{C_2^2 s^2}{R_2} - \frac{C_2^2 s^2}{R_2}$$

$$= \frac{R_1 C_1 s + 1 + R_1 C_2 s + R_1 R_2 C_1 C_2 s^2 + R_2 C_2 s}{R_1 R_2}$$


$$V_2(s) = \frac{\Delta_2(s)}{\Delta(s)} = \frac{R_1 C_1 s V_1(s) + V_1(s) + R_1 C_2 s V_1(s) + R_1 R_2 C_1 C_2 s^2 V_1(s)}{R_1 C_1 s + 1 + R_1 C_2 s + R_1 R_2 C_1 C_2 s^2 + R_2 C_2 s}$$

$$V_2(s) = \left[\frac{R_1 R_2 C_1 C_2 s^2 + (C_1 + C_2) R_1 s + 1}{R_1 R_2 C_1 C_2 s^2 + (R_1 C_1 + R_1 C_2 + R_2 C_2) s + 1} \right] V_1(s)$$

10-39)

10

A)

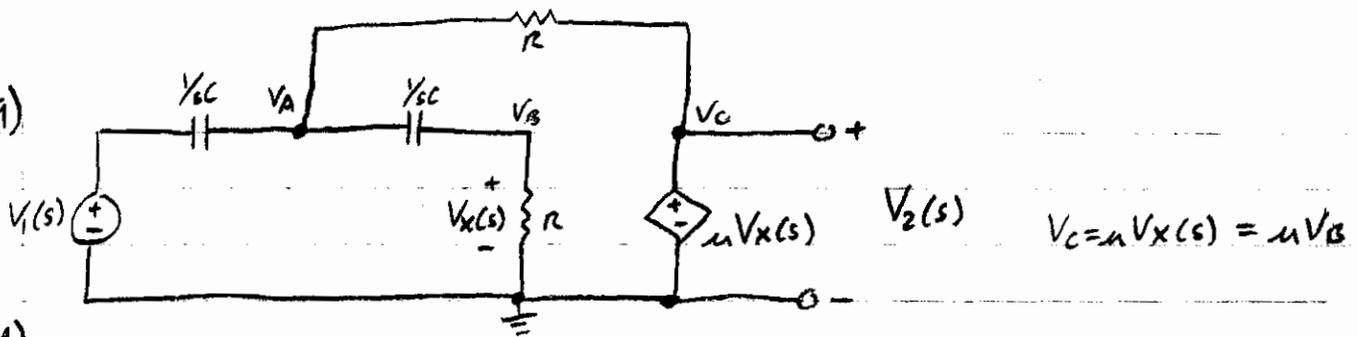

$$\text{Node A: } (Cs + 1/R + Cs)VA - CsVB - \frac{\mu V_B}{R} = CsV_1(s)$$

$$\text{Node B: } (Cs + 1/R)VB - CsVA = 0$$

$$\Delta(s) = \begin{bmatrix} 2Cs + 1/R & -Cs - \frac{\mu}{R} \\ -Cs & Cs + 1/R \end{bmatrix} = 2C^2s^2 + \frac{Cs}{R} + \frac{2Cs}{R} + \frac{1}{R^2} - C^2s^2 - \frac{\mu Cs}{R}$$

$$= \frac{2R^2C^2s^2 + RCs + 2RCs + 1 - R^2C^2s^2 - \mu RCs}{R^2}$$

$$= \frac{R^2C^2s^2 + 3RCs - \mu RCs + 1}{R^2}$$

$$\Delta(s) = \frac{(RCs)^2 + (3-\mu)RCs + 1}{R^2}$$

B) Select R, C, μ so that $\omega_0 = 5k \text{ rad/s}$ and $\zeta = 1/\sqrt{2}$

$$\frac{R^2C^2s^2}{R^2} + \frac{(3-\mu)RCs}{R^2} + \frac{1}{R^2} = C^2s^2 + \frac{(3-\mu)Cs}{R} + \frac{1}{R^2}$$

$$s^2 + 2\zeta\omega_0 s + \omega_0^2 = s^2 + \frac{(3-\mu)s}{RC} + \left(\frac{1}{RC}\right)^2$$

$$\frac{1}{RC} = \omega_0 = 5000 \quad RC = 1/5000 = .0002$$

$$\frac{3-\mu}{RC} = 2\zeta\omega_0 = 2(5000)(1/\sqrt{2}) = 5000\sqrt{2}$$

$$3-\mu = 5000\sqrt{2} (.0002)$$

$$\mu = 1.586$$

$$RC = .0002$$