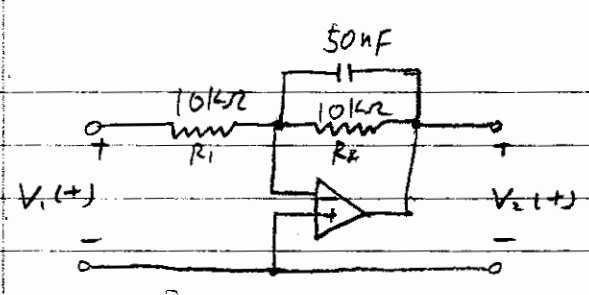


12-4
10




$C = 50\text{nF}$
 $R_1 = R_2 = 10\text{k}\Omega$

$$\bar{Z}_2 = \frac{R_2 \frac{1}{sC}}{R_2 + \frac{1}{sC}} = \frac{R_2}{R_2 sC + 1} \quad Z_1 = R_1 \quad T_V(s) = -\frac{R_2}{R_2 sC + 1} \cdot \frac{1}{R_1} = -\frac{1}{R_1 sC + 1}$$

$$= -\frac{\frac{1}{R_1 C}}{s + \frac{1}{R_1 C}}$$
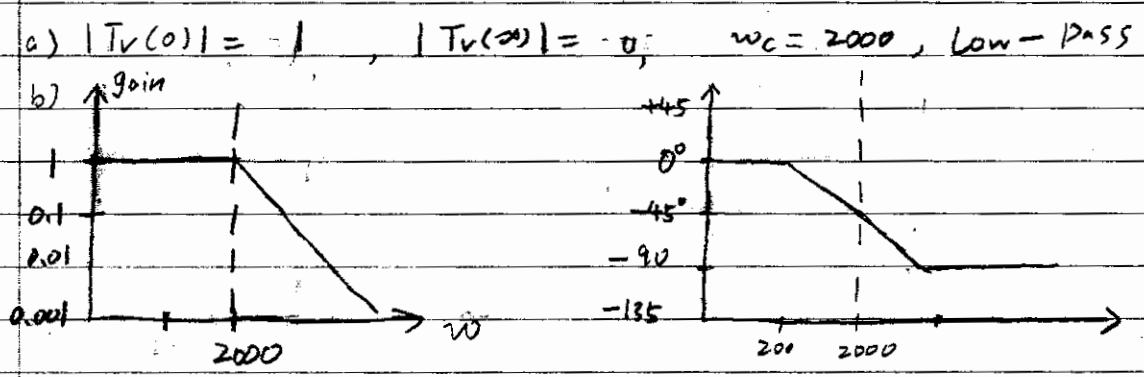
$$\Rightarrow T_V(s) = -\frac{2000}{s + 2000}$$



c) $T_V(s) = -\frac{R_2}{(R_2 sC + 1)R_1} \Rightarrow T_V(s)|_{s=0} = -\frac{R_2}{R_1}$


To double passband gain, either have $R_2 \times 2$ or $R_1 / 2$

$$\Rightarrow T_V(s) = -\frac{R_2/R_1}{\frac{s}{\frac{1}{R_2 C}} + 1}$$

R_2 cannot change b/c it changes ω_c

$$\Rightarrow \text{SO change } R_1 \text{ to } R_1/2 = 10\text{k}\Omega/2 = 5\text{k}\Omega$$

12-15
10

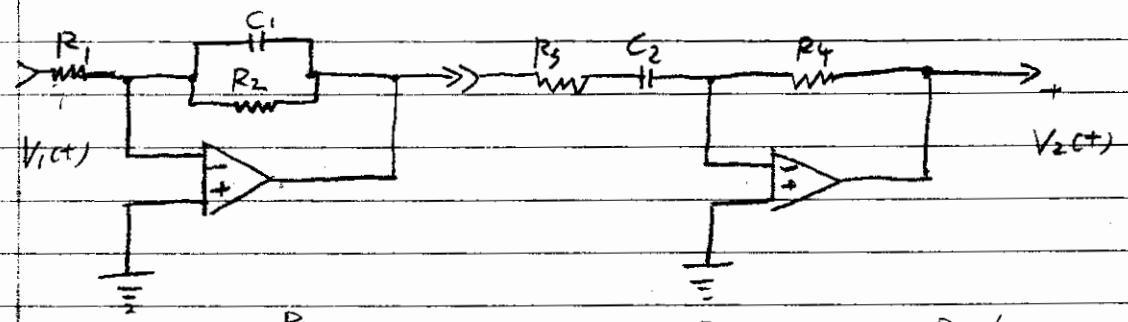

$$\Rightarrow C_1/R_2 = \frac{R_2}{R_2 sC + 1} \Rightarrow T_{V1} = -\frac{R_2}{(R_2 sC + 1)R_1} = -\frac{R_2/R_1}{\frac{s}{\frac{1}{R_2 C}} + 1}$$

→

Select elements values so $K=10$, $\omega_c = 100$ & 2500 rad/s


$$R > 10 \text{ k}\Omega \quad C \leq 1 \text{ nF}$$

$$T_{V_2}(s) = -\frac{R_4}{R_3 + \frac{1}{sC_2}} = -\frac{R_4 C_2 s}{R_3 C_2 s + 1}$$

$$T_V(s) = \left[\frac{R_2}{(R_2 s C_1 + 1) R_1} \right] \cdot \left[\frac{R_4 C_2 s}{R_3 C_2 s + 1} \right]$$

Low Pass $\omega_c = \frac{1}{R_2 C_1}$

High Pass $\omega_c = \frac{1}{R_3 C_2}$

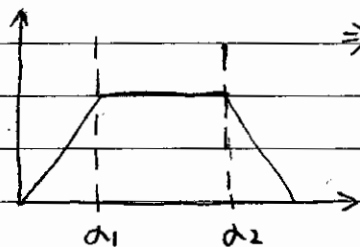

$$\Rightarrow \text{Gain} = \left[\frac{R_2}{R_1} \cdot \frac{R_4}{R_3} \right] = \frac{R_2 R_4}{R_1 R_3} = 10$$

$$\Rightarrow \frac{1}{R_2 C_1} = 2500 \text{ rad/s} \quad \& \quad \frac{1}{R_3 C_2} = 100 \text{ rad/s}$$

Let $C_1 = 1 \text{ nF}$, $C_2 = 20 \text{ nF}$

$$\Rightarrow R_2 = 400 \text{ k}\Omega \quad R_3 = 500 \text{ k}\Omega$$


$$\Rightarrow \text{Gain} = \frac{400 \text{ k} \cdot R_4}{500 \text{ k} \cdot R_1} = 10 \Rightarrow \frac{4R_4}{5R_1} = 10 \Rightarrow \frac{R_4}{R_1} = \frac{25}{2} = \frac{250}{20}$$

So $R_4 = 250 \text{ k}\Omega$, $R_1 = 20 \text{ k}\Omega$, $R_3 = 500 \text{ k}\Omega$, $R_2 = 400 \text{ k}\Omega$
 $C_1 = 1 \text{ nF}$, $C_2 = 20 \text{ nF}$

12-21.

$R=24$ bandwidth = 4 M rad/s , $\omega_c = \omega_0 = 40 \text{ M rad/s}$ $L, C, Q = ?$
 $\omega_1, \omega_2 = ?$

10

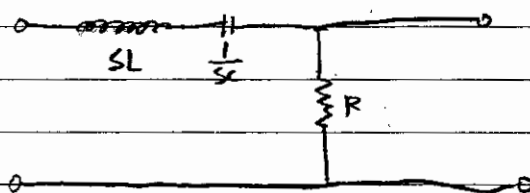

$$\Rightarrow 4 \times 10^6 = \frac{24}{L} \Rightarrow L = 6 \mu\text{H}$$

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow C = \frac{1}{L \omega_0^2} = 104 \text{ pF}$$

$$\Rightarrow Q = \frac{\omega_0}{B} = \frac{40 \times 10^6}{4 \times 10^6} = 10$$

$$\omega_{c1} = 30.05 \text{ M}$$

$$\omega_{c2} = 42.05 \text{ M}$$

11-21 continued

$$\begin{cases} 4\text{M} = \omega_{c2} - \omega_{c1} \\ 40\text{M} = \sqrt{\omega_{c1} \cdot \omega_{c2}} \end{cases} \Rightarrow \begin{cases} 4\text{M} = \omega_{c2} - \omega_{c1} \\ (40\text{M})^2 = \omega_{c1} \cdot \omega_{c2} \end{cases}$$


$$\Rightarrow \omega_{c2} = 4\text{M} + \omega_{c1} \Rightarrow (40\text{M})^2 = \omega_{c1} \cdot (4\text{M} + \omega_{c1})^2$$

$$\omega_{c1} = 38.05 \text{ Mrad/s}$$

$$4\text{M} = \omega_{c2} - 38.05\text{M} \Rightarrow \omega_{c2} = 42.05 \text{ Mrad/s}$$

31.

10

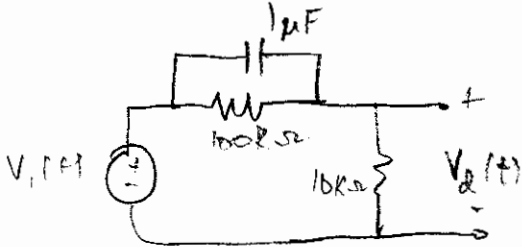

$$T(s) = \frac{10000}{10000 + \left(\frac{1}{10^{-6}s} \cdot 10^5 \right)} = \frac{10^4}{10^4 + \frac{10^5}{10^6 + 10^5 s}}$$


$$= \frac{10^{10} + 10^9 s}{11 \times 10^{10} + 10^9 s} = \frac{s + 10}{s + 110} \quad \begin{matrix} z_1 = -10 \\ p_1 = -110 \end{matrix}$$

$$T(j\omega) = \frac{1}{11} \left(\frac{1 + j\omega/10}{1 + j\omega/110} \right)$$

$$\omega_c = 10 (z_1), 110 (p_1)$$

$$k_b = \frac{1}{11} \quad |T(j\omega)|_{sc} = \frac{1/11 \cdot (4/10)}{\omega/110} = 1$$

$$|T(j\omega)|_{sc} = \begin{cases} 1/11 & 0 < \omega < 10 \\ \omega/110 & 10 < \omega < 110 \\ 1 & \omega > 110 \end{cases}$$

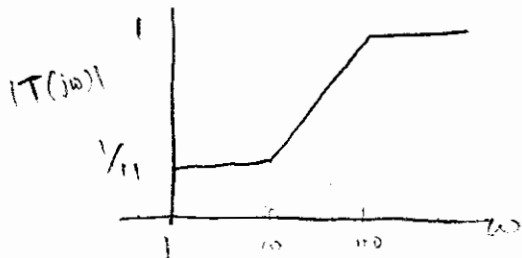

$$v_1 = 10 \sin 30t$$

$$A_{sc} = \frac{30}{110} = 0.273 \text{ V}$$

$$A_{act} = \frac{1}{11} \left| \frac{1 + j \cdot 30/10}{1 + j \cdot 30/110} \right| = 0.2796 \text{ V}$$

