


14-16 Low pass Sallen-Key with $\omega_0 := 2000 \text{ rad/s}$ and $\zeta := 0.5$

Use unity gain method: let $R := 10^4 \Omega$, then

$$C_1 := \frac{1}{\zeta \cdot \omega_0 \cdot R} \quad C_2 := \zeta^2 \cdot C_1 \quad R_1 := R \quad R_2 := R$$

$$R_1 = 1 \times 10^4 \quad \Omega \quad R_2 = 1 \times 10^4 \quad \Omega$$
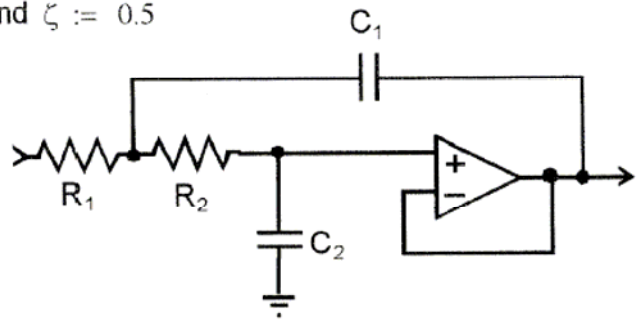
$$C_1 = 1 \times 10^{-7} \quad \text{F} \quad C_2 = 2.5 \times 10^{-8} \quad \text{F}$$




14-19 High pass with $\omega_0 := 2500 \text{ rad/s}$ and $\zeta := 0.75$

Use unity gain method: let $C := 200 \cdot 10^{-9}$, then

$$R_2 := \frac{1}{\zeta \cdot \omega_0 \cdot C} \quad R_1 := \zeta^2 \cdot R_2 \quad C_1 := C \quad C_2 := C$$

$$R_1 = 1.5 \times 10^3 \text{ } \Omega \quad R_2 = 2.667 \times 10^3 \text{ } \Omega$$
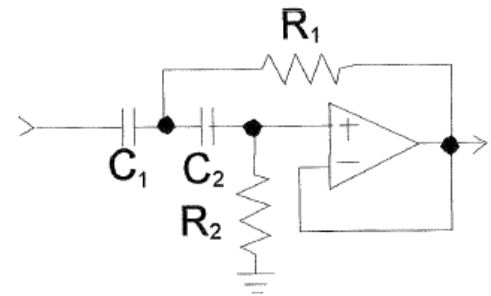
$$C_1 = 2 \times 10^{-7} \text{ F} \quad C_2 = 2 \times 10^{-7} \text{ F}$$



14-31 First-order cascade poles for $\omega_C := 200$; $T_{MAX} := 10^{\frac{0}{20}}$; $T_{MIN} := 10^{\frac{-30}{20}}$; $\omega_{MIN} := 10^3$

$$\alpha(n) := \frac{\omega_C}{\sqrt{2^n - 1}} \quad T(s, n) := \frac{T_{MAX}}{\left(\frac{s}{\alpha(n)} + 1\right)^n} \quad \text{Define Gain}_{dB}(\omega, n) := 20 \cdot \log(|T(j \cdot \omega, n)|)$$

$$n := 3 \quad \text{Gain}_{dB}(\omega_{MIN}, n) = -26.248$$


$$n := 4 \quad \text{Gain}_{dB}(\omega_{MIN}, n) = -30.327 \quad \leftarrow n = 4 \text{ is the lowest order} \quad \alpha(4) = 459.792 \quad T_{MAX} = 1$$

The required T(s) is $T(s) := \frac{1}{\left(\frac{s}{459.792} + 1\right)^4}$

Use a four-stage cascade of identical first-order low-pass voltage divider filters with $K = 1$ and

$$R \cdot C = \frac{1}{459.792}$$

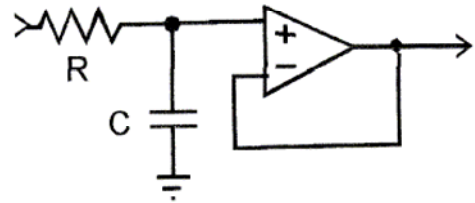Let $R := 10^4 \Omega$ then $C := \frac{1}{R \cdot 459.792} \quad C = 2.175 \times 10^{-7} \text{ F}$



14-32 Butterworth poles for $\omega_C := 200$; $T_{MAX} := 10^{\frac{0}{20}}$; $T_{MIN} := 10^{\frac{-30}{20}}$; $\omega_{MIN} := 10^3$

$$\frac{1}{2} \cdot \frac{\ln \left[\left(\frac{T_{MAX}}{T_{MIN}} \right)^2 - 1 \right]}{\ln \left(\frac{\omega_{MIN}}{\omega_C} \right)} = 2.146 \quad \leftarrow n = 3 \text{ is the lowest order} \quad T(s) = \frac{T_{MAX}}{q_3 \left(\frac{s}{\omega_C} \right)}$$

The required transfer function is $q_3(s) = (s + 1) \cdot (s^2 + s + 1)$ $T_{MAX} = 1$

$$T(s) = \frac{1}{\left(\frac{s}{200} + 1 \right) \cdot \left[\left(\frac{s}{200} \right)^2 + \frac{s}{200} + 1 \right]} = \left(\frac{1}{\frac{s}{200} + 1} \right) \cdot \left[\frac{1}{\left[\left(\frac{s}{200} \right)^2 + \frac{s}{200} + 1 \right]} \right] = T_1(s) \cdot T_2(s)$$

Use a two-stage cascade design

1st stage: Use a first-order low-pass voltage divider with

$$R \cdot C = \frac{1}{200}$$


Let $R := 10^4 \Omega$ then $C := \frac{1}{200R}$ $C = 5 \times 10^{-7} \text{ F}$

2nd stage: Use a 2nd order unity gain S-K design with

$$\omega_0 := 200 \quad \zeta := 0.5 \quad \text{Let} \quad C_1 := 10^{-7} \quad C_2 := \zeta^2 \cdot C_1$$

$$R := \left(\sqrt{C_1 \cdot C_2} \cdot \omega_0 \right)^{-1} \quad R_1 := R \quad R_2 := R$$
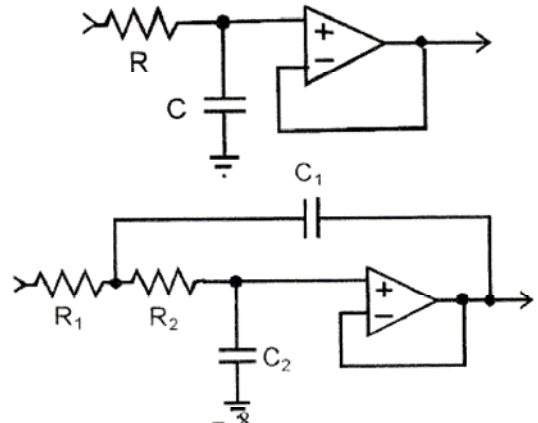
$$R_1 = 1 \times 10^5 \Omega \quad R_2 = 1 \times 10^5 \Omega \quad C_1 = 1 \times 10^{-7} \text{ F} \quad C_2 = 2.5 \times 10^{-8} \text{ F}$$



14-40

$$f_C := 25000 \quad T_{MAX} := 1 \quad T_{MIN} := 10^{-1.5} \quad f_{MIN} := 200 \cdot 10^3$$

Butterworth

$$\frac{1}{2} \frac{\ln \left[\left(\frac{T_{MAX}}{T_{MIN}} \right)^2 - 1 \right]}{\ln \left(\frac{f_{MIN}}{f_C} \right)} = 1.661 \quad \leftarrow n = 2$$

Chebyshev

$$\frac{\operatorname{acosh} \left[\sqrt{\left(\frac{T_{MAX}}{T_{MIN}} \right)^2 - 1} \right]}{\operatorname{acosh} \left(\frac{f_{MIN}}{f_C} \right)} = 1.498 \quad \leftarrow n = 2$$

Since Butterworth & Chebyshev both require $n = 2$, use Butterworth because of easier to design and similar parts

$$\omega_C := 2\pi \cdot f_C$$

$$T(s) = \frac{1}{\left[\left(\frac{s}{\omega_C} \right)^2 + \left(\frac{s}{\omega_C} \right) + 1 \right]} = \frac{1}{\left(\frac{s}{\omega_0} \right)^2 + 2\zeta \left(\frac{s}{\omega_0} \right) + 1}$$

$$\omega_0 := \omega_C \quad \zeta := 0.5$$


use a unity gain design with $\omega_0 = 1.571 \times 10^5$

and $\zeta = 0.5$ Let $C_1 := 10^{-8}$ then $C_2 := \zeta^2 \cdot C_1$

$$R := \left[\left(\sqrt{C_1 \cdot C_2} \right) \cdot \omega_0 \right]^{-1}, \quad R_1 := R, \quad R_2 := R$$

$$C_1 = 1 \times 10^{-8} \text{ F} \quad C_2 = 2.5 \times 10^{-9} \text{ F}$$
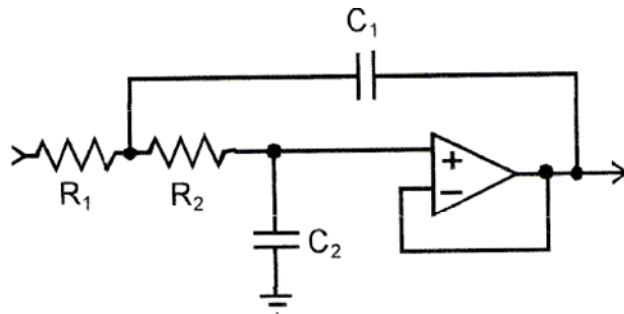
$$R_1 = 1.273 \times 10^3 \text{ } \Omega \quad R_2 = 1.273 \times 10^3 \text{ } \Omega$$



The element values calculated above can be used to verify the design.

Text eq. (14-3) gives the transfer function in terms of circuit elements. With $\mu = 1$ the transfer function is written as

$$T(s) := \frac{1}{R_1 \cdot R_2 \cdot C_1 \cdot C_2 \cdot s^2 + (R_1 \cdot C_1 + R_2 \cdot C_2 + R_1 \cdot C_2 - R_2 \cdot C_1) \cdot s + 1}$$

Testing the gain of the design at 25 kHz and 200 kHz yields

$$20 \log \left(\left| T(j \cdot 2\pi \cdot 25 \cdot 10^3) \right| \right) = 3.857 \times 10^{-15} \quad \leftarrow \text{gain essentially unchanged at 25 kHz}$$

$$20 \log \left(\left| T(j \cdot 2\pi \cdot 200 \cdot 10^3) \right| \right) = -36.056 \quad \leftarrow \text{less than -30 dB at 200 kHz as required}$$