
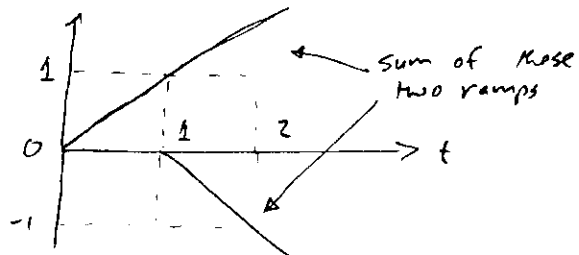


$$1a) \quad x(t) = \delta(t) + 5t u(t) + e^{-10t} \cos(2t) u(t)$$
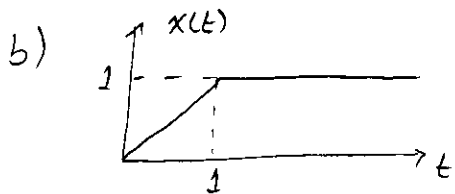
$$X(s) = 1 + \frac{5}{s^2} + \frac{s+10}{(s+10)^2 + 2^2} = 1 + \frac{5}{s^2} + \frac{s+10}{s^2 + 20s + 104}$$



$$x(t) = r(t) - r(t-1)$$

$$= t u(t) - (t-1) u(t-1)$$

$$X(s) = \frac{1}{s^2} - \frac{e^{-s}}{s^2} = \frac{1-e^{-s}}{s^2}$$

$$c) \quad X(s) = \frac{s+2}{s^2+s} = \frac{s+2}{s(s+1)} = \frac{k_1}{s} + \frac{k_2}{s+1}$$

$$\left. \begin{aligned} k_1 &= \frac{s+2}{s+1} \Big|_{s=0} = 2 \\ k_2 &= \frac{s+2}{s} \Big|_{s=-1} = -1 \end{aligned} \right\}$$

$$X(s) = \frac{2}{s} - \frac{1}{s+1}$$

$$x(t) = 2u(t) - e^{-t} u(t)$$

$$d) \quad X(s) = \frac{s+1}{s^2+2s+5}$$

method #1:  $X(s) = \frac{s+1}{(s+1)^2 + 2^2} = e^{-t} \cos(2t) u(t)$

method #2:  $X(s) = \frac{s+1}{(s-(-1-j2))(s-(-1+j2))} = \frac{k}{s+1+j2} + \frac{k^*}{s+1-j2}$

$$k = \frac{s+1}{s+1-j2} \Big|_{s=-1-j2} = \frac{-j2}{-j4} = \frac{1}{2} \quad \text{so} \quad \begin{cases} |k| = \frac{1}{2} \\ \angle k = 0^\circ \\ \alpha = 1 \\ \beta = 2 \end{cases}$$


$$x(t) = 2|k| e^{-\alpha t} \cos(\beta t + \angle k) u(t)$$

$$= e^{-t} \cos(2t) u(t)$$

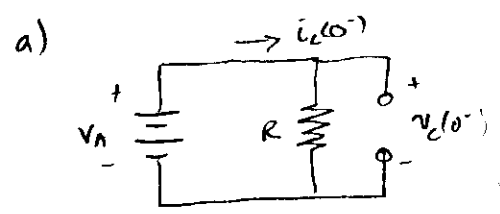2) Using the property that, at steady state,


- inductors  $\leftrightarrow$  shorts
- capacitors  $\leftrightarrow$  open circuits

We can rewrite the block diagrams just before  $t=0$  as follows...




$$v_C(0^-) = V_A$$

$$i_L(0^-) = \frac{V_A}{R}$$

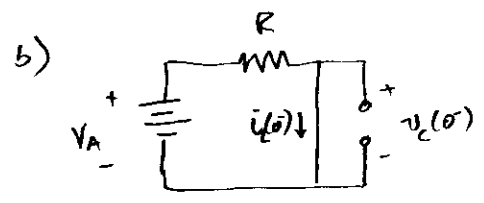

$$v_C(0^-) = 0$$


$$i_L(0^-) = \frac{V_A}{R}$$

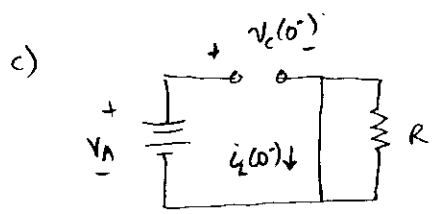

$$v_C(0^-) = V_A$$

$$i_L(0^-) = 0$$

3) method #1:

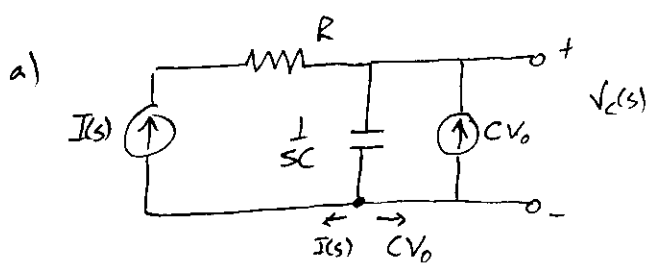


$$I(s) = \frac{1}{s+10}$$

b)

$$v_C(s) = \frac{1}{sC} (I(s) + CV_0) = \frac{1}{sC(s+10)} + \frac{V_0}{s} = \frac{1/C}{s(s+10)} + \frac{V_0}{s}$$

method #2:

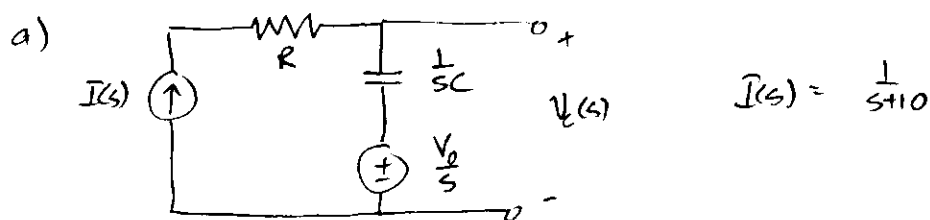

b) 
$$V_c(s) = \frac{V_0}{s} + I(s) \frac{1}{sC} = \frac{V_0}{s} + \frac{1}{(s+10)sC} = \frac{1/C}{s(s+10)} + \frac{V_0}{s}$$

c) To find the forced/natural poles, consider the zero-state transfer function from forced input to output:

$$V_c(s) \Big|_{\text{zero-state}} = \frac{1}{sC} \cdot I(s) = \frac{1/C}{s} \cdot \frac{1}{s+10}$$

forced pole at  $s = -10$   
 natural pole at  $s = 0$

d) 
$$V_c(s) = \frac{1/C}{s(s+10)} + \frac{V_0}{s}$$

$$\frac{1/C}{s(s+10)} = \frac{k_1}{s} + \frac{k_2}{s+10} \quad \left\{ \begin{array}{l} k_1 = \frac{1/C}{s+10} \Big|_{s=0} = \frac{1}{10C} \\ k_2 = \frac{1/C}{s} \Big|_{s=-10} = -\frac{1}{10C} \end{array} \right.$$

$$V_c(s) = \frac{1}{10C} \left( \frac{1}{s} \right) - \frac{1}{10C} \left( \frac{1}{s+10} \right) + \frac{V_0}{s}$$

$$v_c(t) = \left( \frac{1}{10C} + V_0 \right) u(t) - \frac{1}{10C} e^{-10t} u(t)$$



e) Components proportional to the initial condition are zero-input:

$$v_c(t) \Big|_{\text{zero-input}} = V_0 u(t)$$

The rest are zero-state:

$$v_c(t) \Big|_{\text{zero-state}} = \frac{1}{10C} u(t) - \frac{1}{10C} e^{-10t} u(t)$$

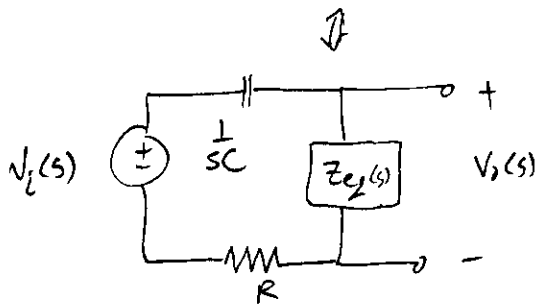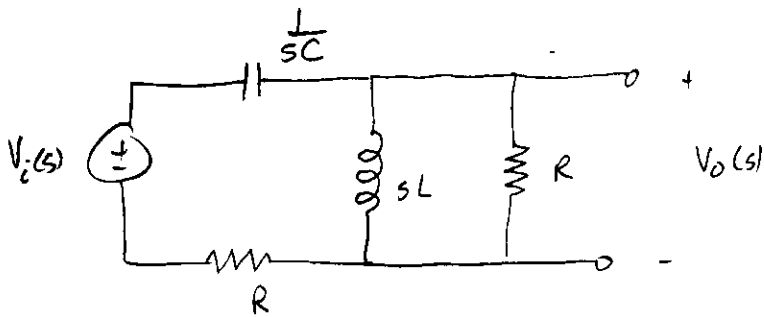4) While it is possible to do a mesh-current or node-voltage analysis, it is much easier to apply voltage division:



$$Z_{eq}(s) = \left( \frac{1}{sL} + \frac{1}{R} \right)^{-1} = \frac{sLR}{sL+R}$$

$$\begin{aligned} V_o(s) &= \frac{Z_{eq}(s)}{\frac{1}{sC} + R + Z_{eq}(s)} = \frac{\frac{sLR}{sL+R}}{\left( \frac{1}{sC} + R \right) + \frac{sLR}{sL+R}} \\ &= \frac{sLR}{\left( \frac{1}{sC} + R \right) (sL+R) + sLR} = \frac{sLR}{\frac{L}{C} + \frac{R}{sC} + sRL + R^2 + sRL} \\ &= \frac{s^2LR}{2s^2RL + s\left(\frac{L}{C} + R^2\right) + \frac{R}{C}} = \frac{s^2/2}{s^2 + s\left(\frac{R^2 + LC}{2LR}\right) + \frac{1}{2LC}} \end{aligned}$$