


ECE 301 MIDTERM #2 SOLUTIONS AU06

1) • Input impedance can be calculated as

$$Z_{in}(s) = \frac{V_{in}(s)}{I_{in}(s)} \quad \text{where} \quad \begin{array}{c} I_{in}(s) \rightarrow \\ \text{---} \oplus \text{---} \\ \text{---} \ominus \text{---} \\ \text{---} \text{ckt} \text{---} \\ \text{---} \text{---} \end{array}$$



Approach: Solve for $I_{in}(s)$ in terms of general $V_{in}(s)$

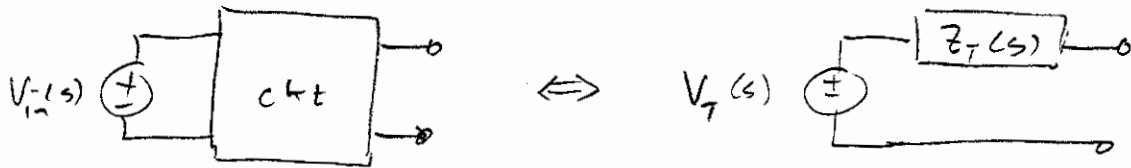• Output impedance is equivalent to the Thevenin impedance:



Approach: Calculate $Z_T(s)$ assuming general $V_{in}(s)$

• But remember Op-Amps behave like:

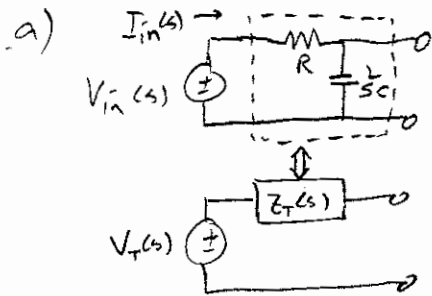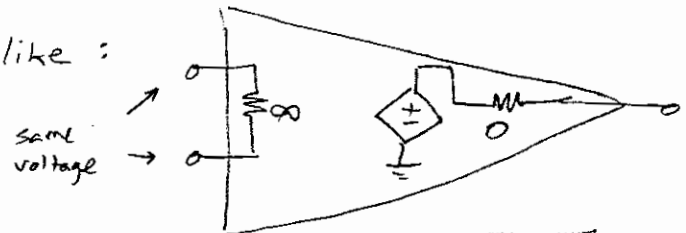


$$I_{in}(s) = \frac{V_{in}(s)}{R + \frac{1}{sC}} \Rightarrow Z_{in}(s) = \frac{V_{in}(s)}{I_{in}(s)} = \boxed{R + \frac{1}{sC}}$$

$$Z_T(s) = \frac{V_{oc}(s)}{I_{sc}(s)} = \boxed{\frac{R}{1 + sRC}} \quad \text{since}$$



$$V_{oc}(s) = V_{in}(s) \frac{1/sC}{1/sC + R} = V_{in}(s) \frac{1}{1 + sRC}$$

$$I_{sc}(s) = \frac{V_{in}(s)}{R}$$

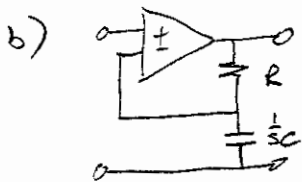


We've discussed this "non-inverting configuration" many times, which has $Z_{in}(s) = \infty$ and $Z_{out}(s) = 0$

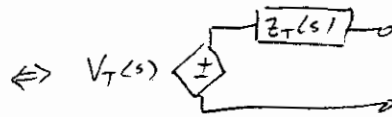
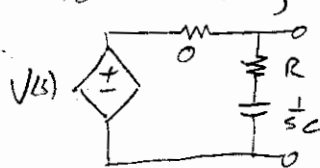
To see why R and C don't affect $Z_{out}(s)$, consider




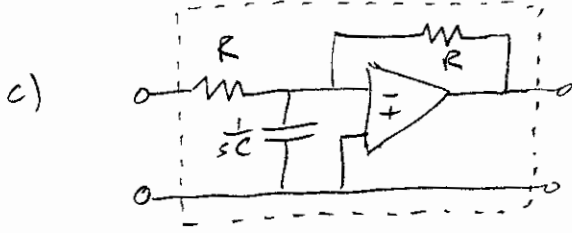
$$\left. \begin{array}{l} V_{oc}(s) = V(s) \\ I_{sc}(s) = \frac{V(s)}{0} = \infty \end{array} \right\} Z_T(s) = \frac{V_{oc}(s)}{I_{sc}(s)} = 0 \quad \checkmark$$



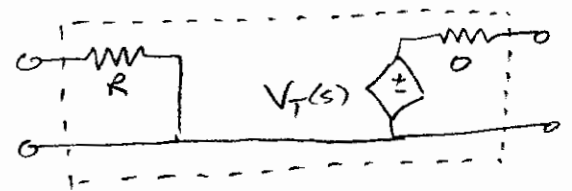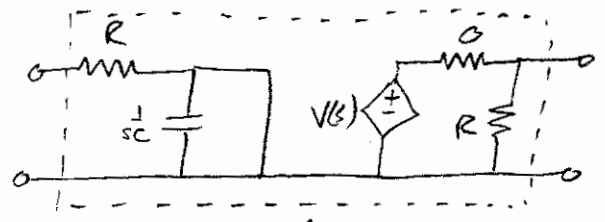Realizing that the input terminals are at the same voltage



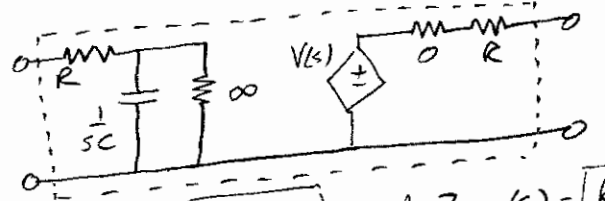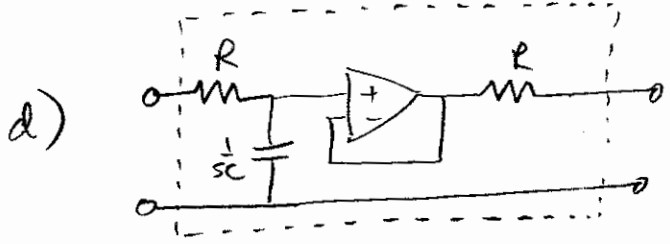Thus $Z_{in}(s) = R$ and $Z_{out}(s) = 0$



Thus $Z_{in}(s) = R + \frac{1}{sC}$ and $Z_{out}(s) = R$

2) Impulse response $e^{-2t} u(t) \xleftrightarrow{\mathcal{L}} \frac{1}{s+2}$
 In other words $\underbrace{Y(s)}_{\frac{1}{s+2}} = T(s) \underbrace{X(s)}_1$, so that $T(s) = \frac{1}{s+2}$

a) The steady state response to $10 \cos(5t)$ equals

$10 |T(j5)| \cos(5t + \angle T(j5))$, where

$$|T(j5)| = \left| \frac{1}{j5+2} \right| = \frac{1}{\sqrt{5^2+2^2}} = \frac{1}{\sqrt{29}} = 0.186$$


$$\angle T(j5) = \angle \left(\frac{1}{j5+2} \right) = -\angle(j5+2) = -\tan^{-1}\left(\frac{5}{2}\right) = -68.2^\circ$$

$= 1.86 \cos(5t - 68.2^\circ)$

b) Step response: $G(s) = T(s) \frac{1}{s} = \frac{1}{s(s+2)} = \frac{k_1}{s} + \frac{k_2}{s+2}$
 Cover-up yields $k_1 = \frac{1}{2}$ & $k_2 = -\frac{1}{2}$, so that

$g(t) = \left[\frac{1}{2} - \frac{1}{2} e^{-2t} \right] u(t)$

3a)

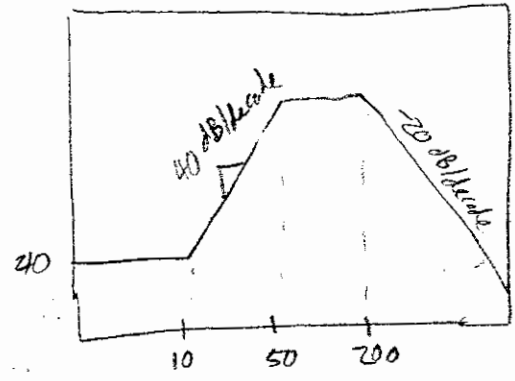

So { two zeros @ $\omega=10$
 two poles @ $\omega=50$
 one pole @ $\omega=200$
 DC gain = 40dB = 100

$$\Rightarrow T(s) = \frac{100 \left(\frac{s}{10} + 1\right)^2}{\left(\frac{s}{50} + 1\right)^2 \left(\frac{s}{200} + 1\right)}$$

|| note that $\left(\frac{s}{\alpha} + 1\right)$ has DC gain = 1, thus 100 appears in numerator.
 || whereas $(s + \alpha)$ does not have DC gain = 1 (unless $\alpha=1$) !



b)

$$T(s) = \frac{s + 200}{5s + 100}$$

$$= \frac{200 \left(\frac{s}{200} + 1\right)}{100 \left(\frac{5s}{100} + 1\right)}$$

$$= 2 \frac{\left(\frac{s}{200} + 1\right)}{\left(\frac{s}{20} + 1\right)}$$

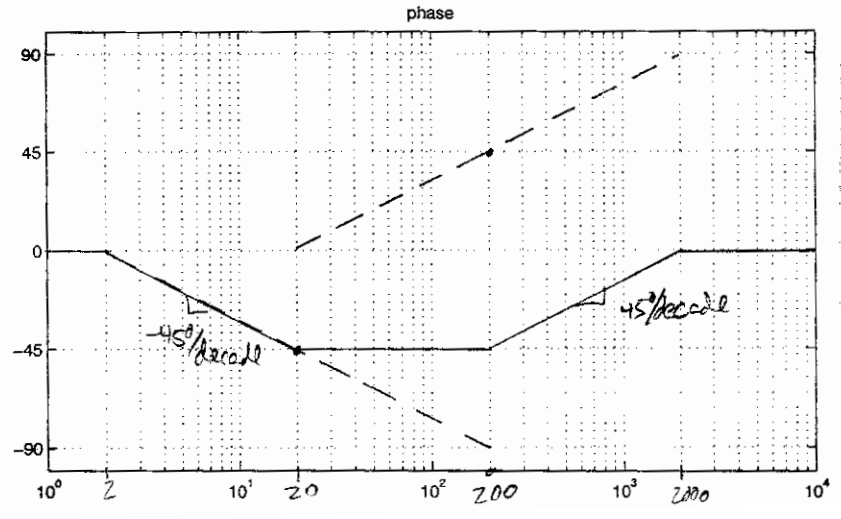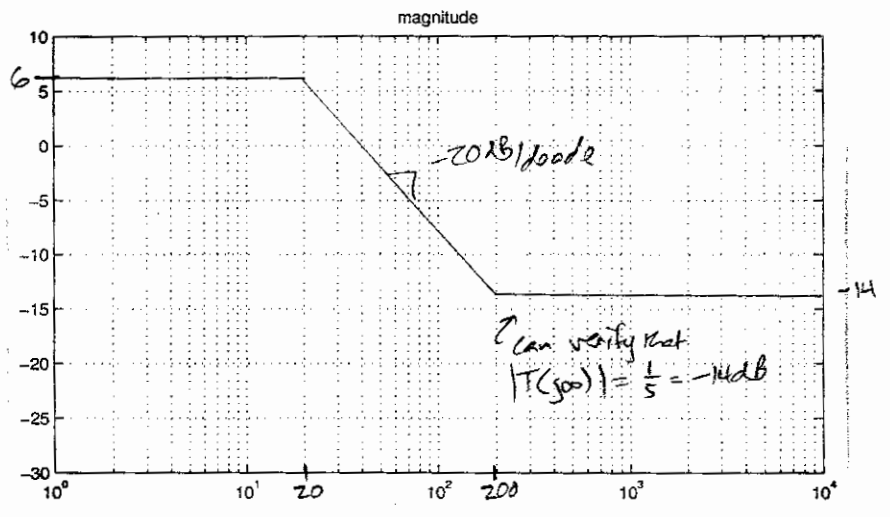So { DC gain = 2 = 6dB
 zero at $\omega=200$
 pole at $\omega=20$



4) These were a few designs that implemented $-\frac{1}{10} \cdot \frac{s+10}{s+1}$ using a single op-amp, no inductors, and 1μF capacitors.

i) $-\frac{1}{10} \cdot \frac{s+10}{s+1} = -\frac{\frac{s}{10} + 1}{s+1} = -\frac{\frac{1}{10} + \frac{1}{s}}{1 + \frac{1}{s}} = -\frac{\frac{10^6}{10} + \frac{10^6}{s}}{\frac{10^6}{10^6} + \frac{10^6}{s}} = \frac{10^5 + \frac{1}{10^{-6}s}}{10^6 + \frac{1}{10^{-6}s}} = -\frac{Z_2(s)}{Z_1(s)}$ for inverting config

$10^6 = 1M$
 $10^5 = 100k$

ii) $-\frac{1}{10} \cdot \frac{s+10}{s+1} = -\frac{1}{10} \cdot \frac{(s+1)^{-1}}{(s+10)^{-1}} = -\frac{1}{10} \cdot \frac{[(\frac{1}{s})^{-1} + (1)^{-1}]^{-1}}{[(\frac{1}{s})^{-1} + (\frac{1}{10})^{-1}]^{-1}} = -\frac{[(\frac{1}{10^{-6}s})^{-1} + (\frac{1}{10^6})^{-1}]^{-1}}{[(\frac{1}{10^{-6}s})^{-1} + (\frac{1}{10 \cdot 10^6})^{-1}]^{-1}} \cdot \frac{1}{10} = -\frac{[(\frac{1}{10^6 s})^{-1} + (10^6)^{-1}]^{-1}}{[(\frac{1}{10^6 s})^{-1} + (10^5)^{-1}]^{-1}} \cdot \frac{1}{10}$

inverting voltage divider

for any R

→ note: must cascade with op-amp first!

iii) $-\frac{s+10}{10s+10} = \frac{1 + \frac{10}{s}}{10 + \frac{10}{s}} = \frac{1 + \frac{10}{s}}{9 + (1 + \frac{10}{s})} = \frac{10^5 + \frac{10^6}{s}}{9 \times 10^5 + (10^5 + \frac{10^6}{s})}$

for any R

iv) $-\frac{s+10}{10} = -\frac{0.1 + s^{-1}}{s^{-1}} = \frac{1}{s+1} = \frac{s^{-1}}{1+s^{-1}} = \frac{10^6 s^{-1}}{10^6 + 10^6 s^{-1}}$

Note: the output impedances of the last two designs are extremely high, hence these are "unfriendly" circuits. The first and simplest design is the "friendliest"!